
CSE 431 Computer Architecture Fall 2015

Chapter 4A: The Single Cycle Processor

Mary Jane Irwin (www.cse.psu.edu/~mji)


[Adapted from *Computer Organization and Design, 5th Edition*,
Patterson & Hennessy, © 2014, Morgan Kaufmann]

Reminders

- ❑ This lecture
 - MIPS datapath and control, PH 4.1-4.4
- ❑ Next lecture
 - MIPS pipelined datapaths, data hazards, PH 4.5-4.7
- ❑ Reminders
 - HW2 is due Sept 17th (our first using SimpleScalar)
 - Quiz 2 will open Sept 9th and will close midnight Sept 22nd
 - Attend one of the unix + SimpleScalar tutorial sessions in the lab (218 IST) Sept 9th and 10th from 7:30 to 9pm
 - First evening midterm exam scheduled
 - Tuesday, **October 6th**, 20:15 to 22:15, Location 22 Deike
 - **I should have heard from all who have conflicts by now**

The Processor: Datapath & Control

- ❑ Our implementation of the MIPS is simplified
 - memory-reference instructions: **lw, sw**
 - arithmetic-logical instructions: **add, sub, and, or, slt**
 - control flow instructions: **beq, j**
- ❑ Generic implementation
 - use the program counter (PC) to supply the instruction address and fetch the instruction from memory (and update the PC)
 - decode the instruction (and read registers)
 - execute the instruction
- ❑ All instructions (except **j**) use the (integer) ALU after reading the registers

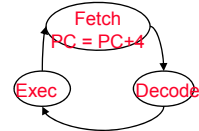


How is the ALU used?

memory-reference? arithmetic? control flow?

Abstract Implementation, First Version

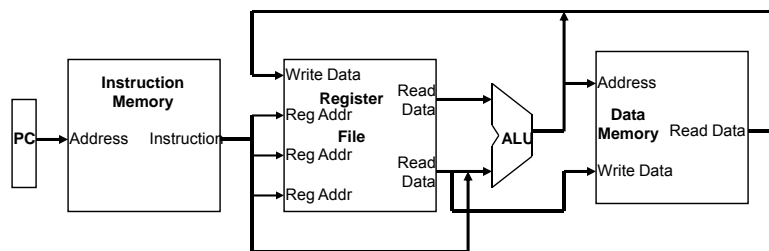
- ❑ Two types of functional units:
 - elements that operate on data values (combinational)
 - elements that contain state (sequential)



- ❑ Single cycle operation
- ❑ Split memory model – one memory for instructions (really L1I\$) and one memory (really L1D\$) for data

Aside: Clocking Methodologies

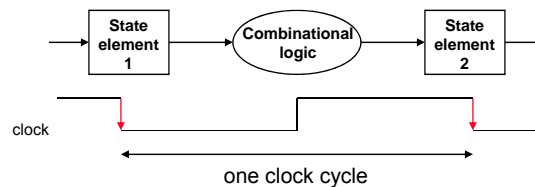
- ❑ The **clocking methodology** defines when data in a state element is valid and stable relative to the clock
 - State elements – a memory element such as a register
 - Edge-triggered – all state changes occur on a clock edge
- ❑ Typical execution
 - read contents of state elements -> send values through combinational logic -> write results to one or more state elements



- ❑ Assumes state elements are written on every clock cycle; if not, need explicit write control signal
 - write occurs only when **both** the write control is asserted and the clock edge occurs

Fetching Instructions

 - ❑ Fetching instructions involves
 - reading the instruction from the Instruction Memory
 - updating the PC value to be the address of the next (sequential) instruction




- PC is updated every clock cycle, so it does not need an explicit write control signal just a clock signal
- Reading from the Instruction Memory is a combinational activity, so it doesn't need an explicit read control signal

Decoding Instructions

□ Decoding instructions involves

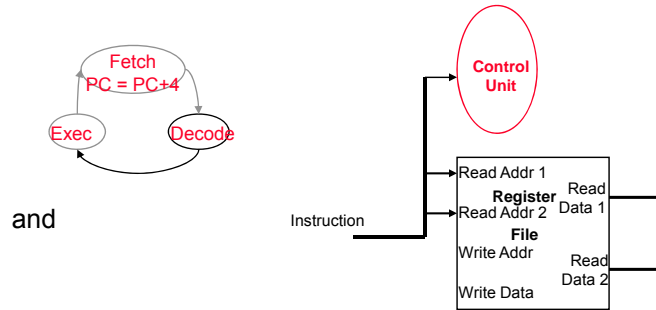- sending the fetched instruction's opcode and function field bits to the control unit




- reading two values from the RF


- RF addresses are contained in the instruction
- Can read registers before the instruction is fully decoded, then ignore what you don't need. Benefits? Costs?

Executing R Format Operations

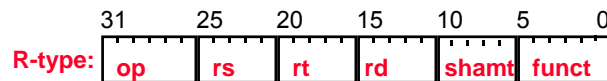□ R format operations (add, sub, slt, and, or)



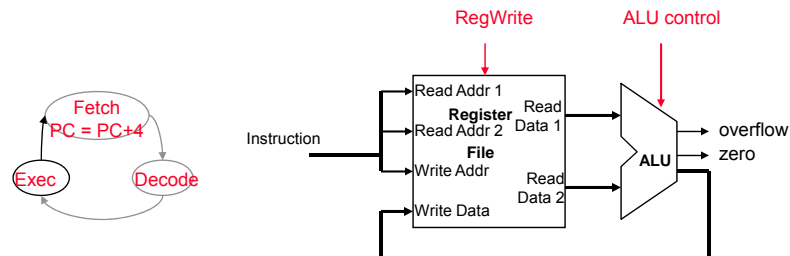- perform operation (op and funct) on values in rs and rt
- store the result back into the RF (into location rd)




- Note that RF is not written every cycle (e.g., sw), so we need an explicit write control signal (RegWrite) for RF

Irwin, PSU, 2015

Irwin, PSU, 2015

Executing Jump Operations

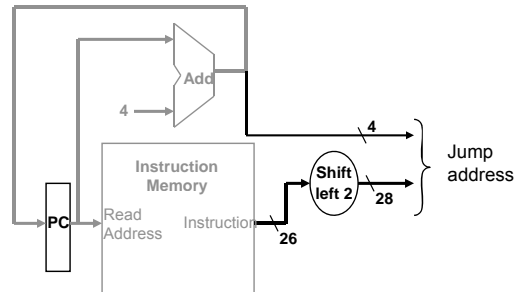- ❑ Jump operation involves
 - replace the lower 28 bits of the PC with the lower 26 bits of the fetched instruction shifted left by 2 bits



Creating a Single Datapath from the Parts


- ❑ Assemble the datapath segments and add control lines and **multiplexors** as needed
- ❑ **Single cycle** design – fetch, decode and execute each instructions in **one** clock cycle
 - no datapath resource can be used more than once per instruction, so some must be duplicated (e.g., separate Instruction Memory and Data Memory, several adders)
 - **multiplexors** needed at the input of shared elements with control lines to do the selection
 - write signals to control writing to the RF and Data Memory
- ❑ Cycle time is determined by length of the longest path

Adding the Control


- Selecting the operations to perform (ALU, RF and Memory read/write)
- Controlling the flow of data (multiplexor inputs)

Observations

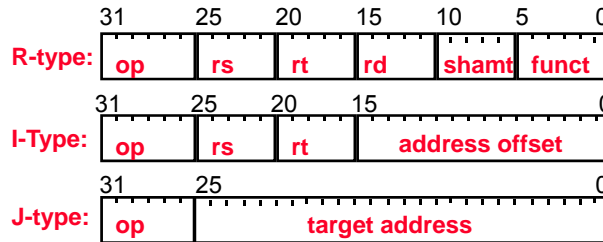- op field **always** in bits 31-26
- addr of registers to be read are **always** specified by the rs field (bits 25-21) and rt field (bits 20-16); for lw and sw rs is the base register
- addr. of register to be written is in one of **two** places – in rt (bits 20-16) for lw; in rd (bits 15-11) for R-type instructions
- offset for beq, lw, and sw **always** in bits 15-0



Single Cycle Datapath with Control Unit

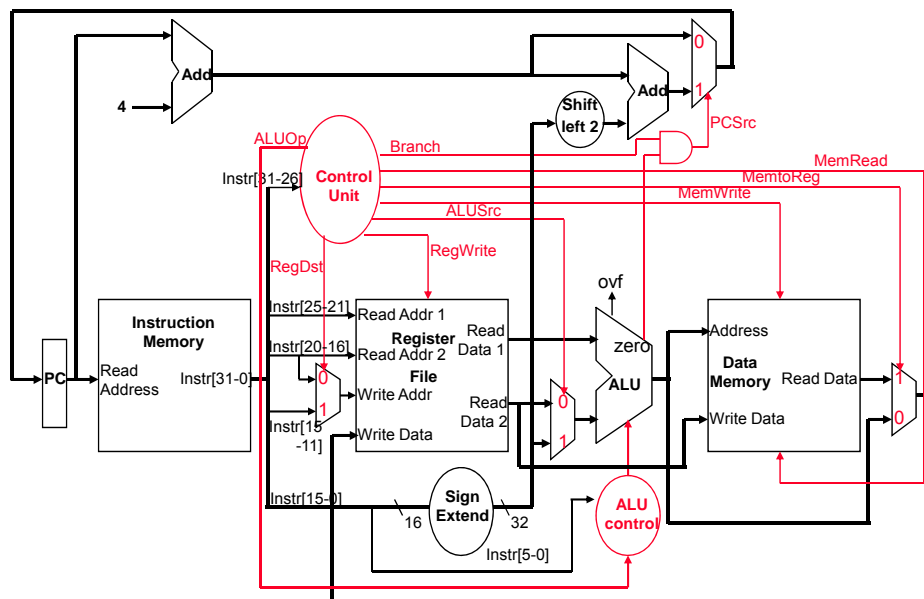


R-type Instruction Data/Control Flow




Irwin, PSU, 2015

Load Word Instruction Data/Control Flow

 

Irwin, PSU, 2015


Store Word Instruction Data/Control Flow

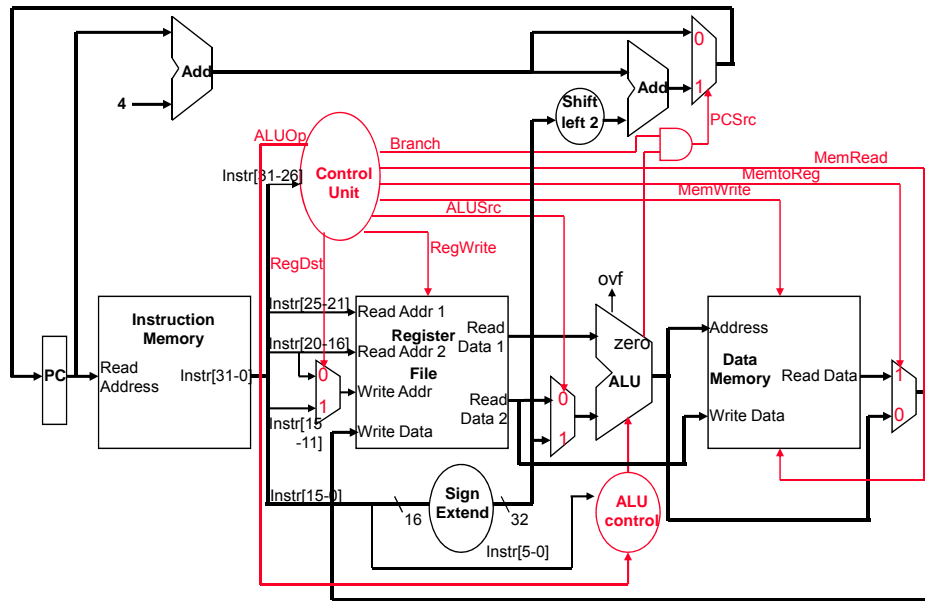

CSE431 Chapter 4A.18


Irwin, PSU, 2015

Branch Instruction Data/Control Flow

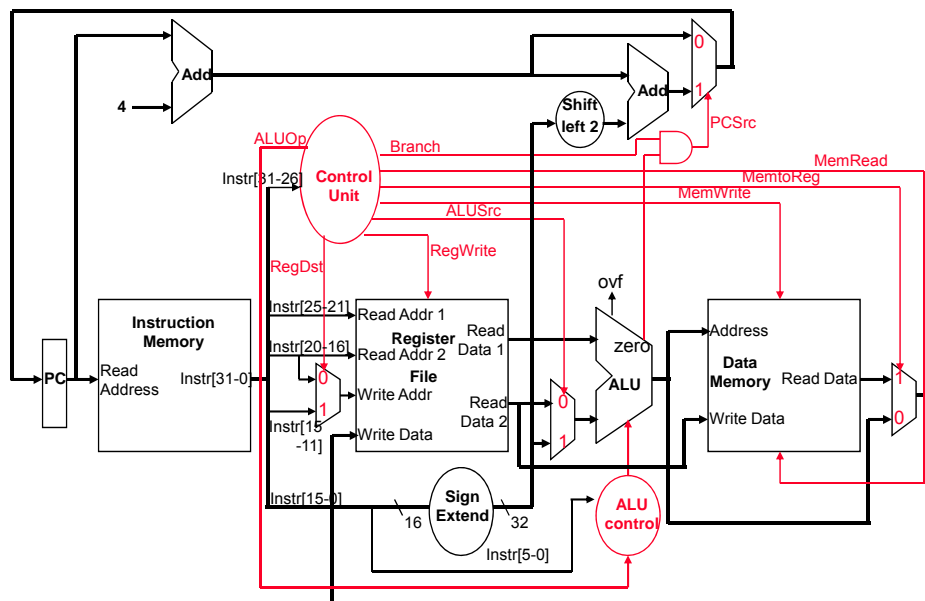

CSE431 Chapter 4A.20

Irwin, PSU, 2015

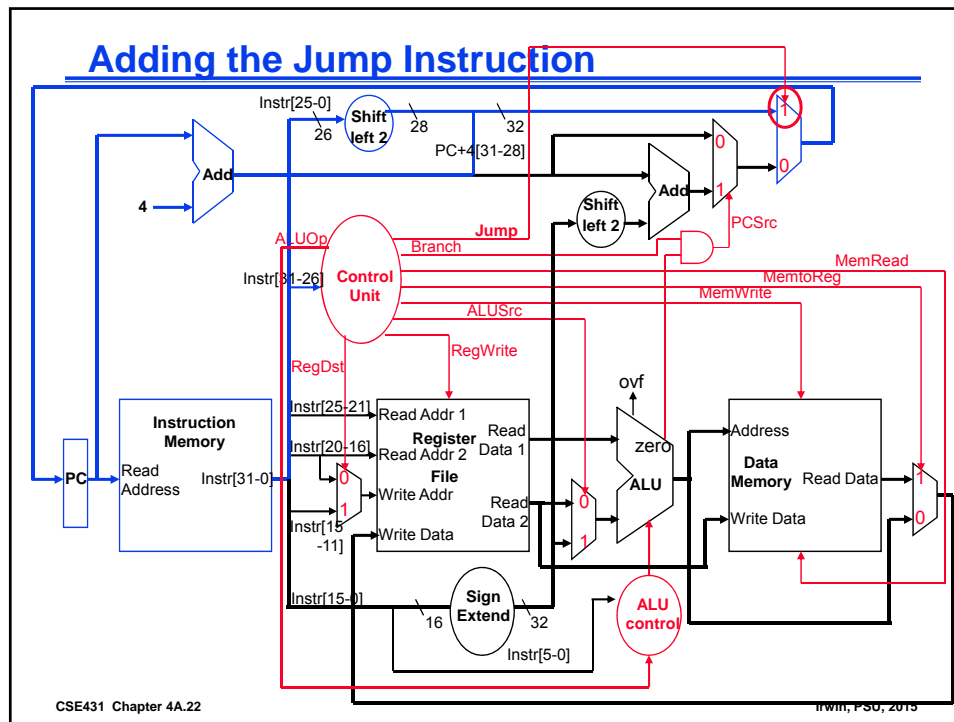

Instruction Times (Critical Paths)


❑ What is the clock cycle time assuming negligible delays for muxes, control unit, sign extend, PC access, shift left 2, wires, setup and hold times except:

- Instruction and Data Memory (200 ps)
- ALU and adders (200 ps)
- Register File access (reads or writes) (100 ps)

Instr.	I Mem	Reg Rd	ALU Op	D Mem	Reg Wr	Total
R-type						
load						
store						
beq						
jump						

Single Cycle Disadvantages & Advantages

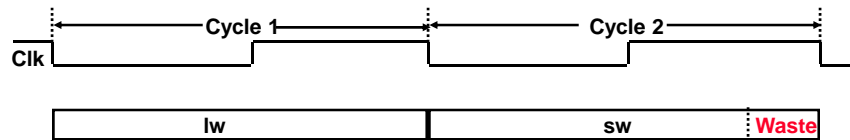- ❑ Uses the clock cycle inefficiently – the clock cycle must be timed to accommodate the **slowest** instruction
 - especially problematic for more complex instructions like floating point multiply




- ❑ May be wasteful of area since some functional units (e.g., adders) must be duplicated since they can not be shared during a clock cycle
- but
- ❑ Is simple and easy to understand

How Can We Make It Faster?

- ❑ Start fetching and executing the next instruction before the current one has completed
 - **Pipelining** – (all?) modern processors are pipelined for performance
 - Remember *the* performance equation:
$$\text{CPU time} = \text{CPI} * \text{CC} * \text{IC}$$
- ❑ Under *ideal* conditions and with a large number of instructions, the speedup from pipelining is approximately equal to the number of pipe stages
 - A five stage pipeline is nearly five times faster because the CC is nearly five times faster
- ❑ Fetch (and execute) more than one instruction at a time
 - Superscalar processing – stay tuned



The Five Stages of Load Instruction

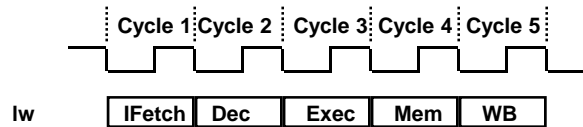

IFetch: Instruction Fetch and Update PC

Dec: Registers Fetch and Instruction Decode

Exec: Execute R-type; calculate memory address


Mem: Read/write the data from/to the Data Memory

WB: Write the result data into the register file

- ❑ Single cycle – each stage is used once in each cycle
 - One active instruction per cycle (a looonng cycle)
- ❑ Pipelined – each stage is used in each cycle
 - Multiple active instructions per cycle (a short cycle)

A Pipelined MIPS Processor

 
- ❑ Start the **next** instruction before the current one has completed
 - improves **throughput** - total amount of work done in a given time
 - instruction **latency** (execution time, delay time, response time - time from the start of an instruction to its completion) is *not* reduced and may increase slightly




- clock cycle (pipeline stage time) is limited by the **slowest** stage
 - for some stages don't need the whole clock cycle (e.g., WB)
- for some instructions, some stages are **wasted** cycles (i.e., nothing is done during that cycle for that instruction)

Single Cycle versus Pipeline

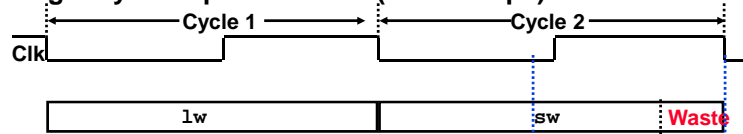Single Cycle Implementation (CC = 800 ps):



Pipeline Implementation (CC = 200 ps):

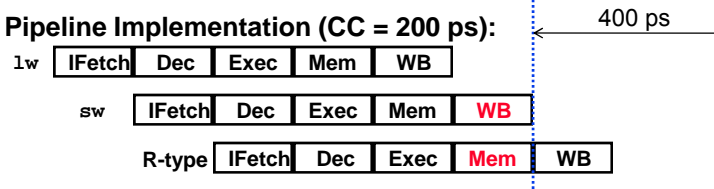


- ❑ To complete an entire instruction in the pipelined case takes 1000 ps (as compared to 800 ps for the single cycle case). Why ?
- ❑ How long does each take to complete 1,000,000 adds ?

Pipelining the MIPS ISA – What Makes It Easy?

- ❑ All instructions are the same length (32 bits)
 - can fetch in the 1st stage and decode in the 2nd stage
- ❑ Only a few instruction formats (three) with **symmetry** across formats
 - can begin reading register file in 2nd stage (before instruction is fully decoded) even if it turns out we don't need it
- ❑ Memory operations occur only in loads and stores
 - can use the execute stage to calculate memory addresses
- ❑ Each instruction writes at most one result (i.e., changes the machine state) and does it in the last few pipeline stages (MEM or WB)
- ❑ Operands must be aligned in memory so a single data transfer takes only one data memory access

MIPS Pipeline Datapath Additions/Mods

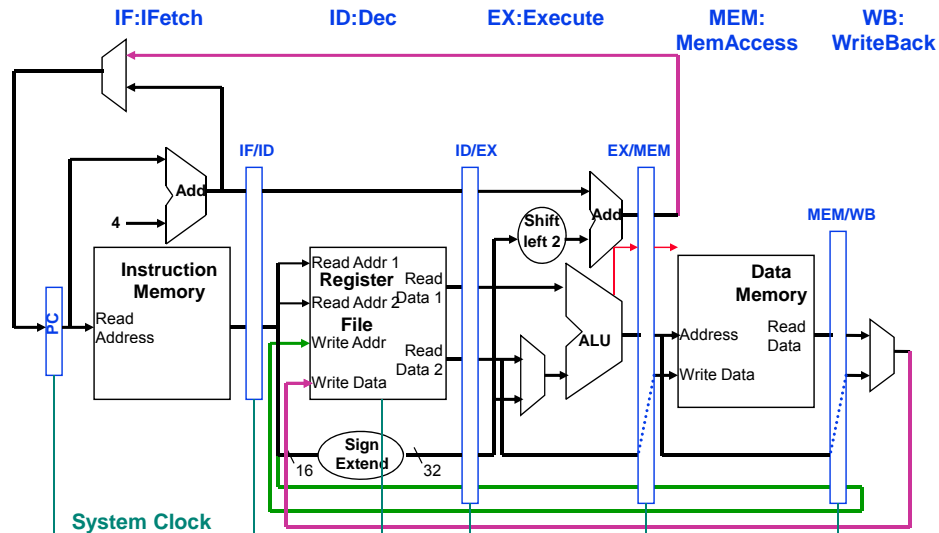- State registers between each pipeline stage to **isolate** them



CSE431 Chapter 4A.31

Irwin, PSU, 2015

Pipeline Control

- IF Stage: read Instr Memory (always asserted) and write PC (on System Clock)
- ID Stage: decoding so no control signals ready yet


	EX Stage				MEM Stage			WB Stage	
	Reg Dst	ALU Op1	ALU Op0	ALU Src	Brch	Mem Read	Mem Write	Reg Write	Mem toReg
R	1	1	0	0	0	0	0	1	0
lw	0	0	0	1	0	1	0	1	1
sw	X	0	0	1	0	0	1	0	X
beq	X	0	1	0	1	0	0	0	X

CSE431 Chapter 4A.32


Irwin, PSU, 2015

MIPS Pipeline Control Path Modifications

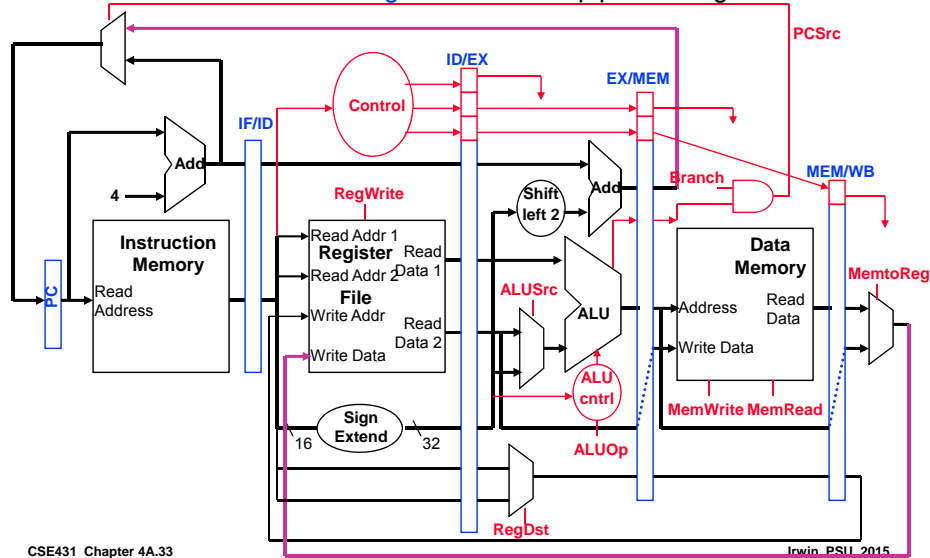- ❑ All control signals can be determined during Decode
 - and held in the **state registers** between pipeline stages




Graphically Representing MIPS Pipeline

 

- ❑ Can help with answering questions like:
 - How many cycles does it take to execute this code?
 - What is the ALU doing during cycle 4?
 - Is there a hazard, why does it occur, and how can it be fixed?

Why Pipeline? For Performance!

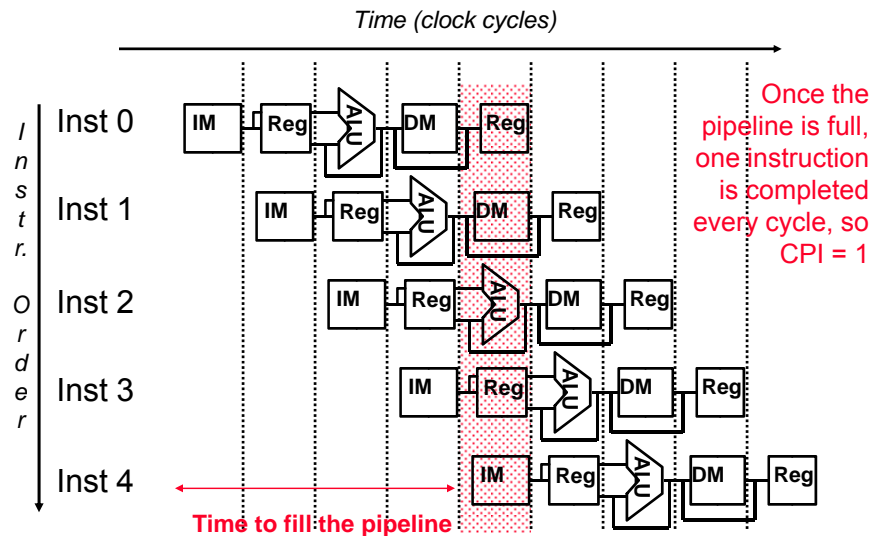

CSE431 Chapter 4A.35

Irwin, PSU, 2015

Pipelining the MIPS ISA – What Makes It Hard?

□ Pipeline Hazards

- **structural hazards**: attempt to use the same resource by two different instructions at the same time
- **data hazards**: attempt to use data before it is ready
 - An instruction's source operand(s) are produced by a prior instruction still in the pipeline
- **control hazards**: attempt to make a decision about program control flow before the condition has been evaluated and the new PC target address calculated
 - branch and jump instructions, exceptions

□ Dependencies backward in time cause hazards

□ Can usually resolve hazards by waiting


- pipeline control must **detect** the hazard
- and take action to **resolve** hazards

CSE431 Chapter 4A.36

Irwin, PSU, 2015

Other Pipeline Structures Are Possible

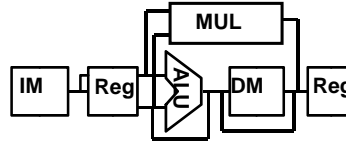- ❑ What about the (slow) multiply operation?
 - Make the clock twice as slow or ...
 - let it take two cycles (since it doesn't use the DM stage)



- ❑ What if the data memory access is twice as slow as the instruction memory?
 - make the clock twice as slow or ...
 - let data memory access take two cycles (and keep the same clock rate)



Summary

- ❑ All modern day processors use pipelining
- ❑ Pipelining doesn't help the **latency** of any single instruction, it helps the **throughput** of the entire workload
- ❑ Potential speedup: a CPI of 1 and fast a CC
- ❑ Pipeline rate limited by **slowest** pipeline stage
 - Unbalanced pipe stages makes for inefficiencies
 - The time to "**fill**" the pipeline and the time to "**drain**" it can impact speedup for deep pipelines and short code runs which occur when there are a lot of branch instructions
- ❑ Must detect and resolve hazards
 - Stalling negatively affects CPI (makes CPI less than the ideal of 1)

Reminders

□ Next lecture

- MIPS pipelined datapaths, data hazards, PH 4.5-4.7

□ Reminders

- HW2 is due Sept 17th (our first using SimpleScalar)
- Quiz 2 will open Sept 9th and will close midnight Sept 22nd
- Attend one of the unix + SimpleScalar tutorial sessions in the lab (218 IST) Sept 9th and 10th from 7:30 to 9pm
- First evening midterm exam scheduled
 - Tuesday, **October 6th**, 20:15 to 22:15, Location 22 Deike
 - **I should have heard from all who have conflicts by now**